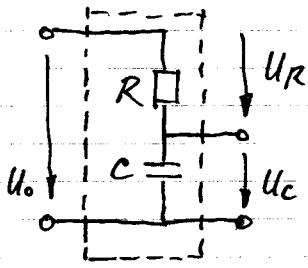


#### 4<sup>th</sup> Exercise:



Consider a series connection of an electrical condenser with capacity  $C$  and a resistor  $R$ . Let the voltage  $U_0 = U_0(t)$ . Our goal is to determine the output signal  $U_c = U_c(t)$ .

(a) There holds:  $U_0 = U_R + U_c$ ,  $U_R = R \cdot I$ ,  $I = Q'$ ,  $Q = C \cdot U_c$

Set up the differential equation for  $U_c$

(b) Let  $U_0(t) = \delta(t - t_0)$ . Determine by means of Laplace-transform the function  $K: [0, \infty) \rightarrow \mathbb{R}$  with:  $U_c(t) = K(t - t_0)$  for  $t \geq t_0 > 0$ .  $K$  is called "pulse response".

(c) Show that  $U_c(t) = U_0(t) * K(t)$ .

(d) Compute  $U_c(t)$  for  $R = 10 \text{ k}\Omega$ ,  $C = 100 \mu\text{F}$  and  $U_0(t) = \cos(\omega t)$ .

4<sup>th</sup> Exercise: <sup>given.</sup>  $U_0(t) = U_R(t) + U_C(t) = R \cdot I(t) + U_C =$   
 (a)  $= R \cdot Q'(t) + U_C(t) = R \cdot C \cdot U_C'(t) + U_C(t).$

(b) Apply the Laplace-transform on DE in (a): with initial cond:  $U_C(0) = U_C'(0) = 0.$

$$R \cdot C \cdot s \cdot (\mathcal{L} U_C)(s) + (\mathcal{L} U_C)(s) = (\mathcal{L} U_0)(s).$$

$$\Leftrightarrow (\mathcal{L} U_C)(s) = (\mathcal{L} U_0)(s) \cdot \frac{1}{RCs + 1} = (\mathcal{L} U_0)(s) \cdot \frac{1}{RC} \cdot \frac{1}{s + \frac{1}{RC}} =$$

$$= (\mathcal{L} U_0)(s) \cdot \mathcal{L} \left( \frac{1}{RC} \cdot e^{-\frac{t}{RC}} \right)(s). \quad (*) \quad \text{transfer function.}$$

• The Laplace-transform of  $U_0(t) = \delta(t - t_0)$  is  $(\mathcal{L} U_0)(s) = e^{-t_0 s}$ , s. 7.0  
 Def 9.23.

put it into (\*)  $\Rightarrow (\mathcal{L} U_C)(s) = e^{-t_0 s} \cdot \mathcal{L} \left( \frac{1}{RC} \cdot e^{-\frac{t}{RC}} \right)(s).$

shifting Theorem  $\Rightarrow U_C(t) = \begin{cases} 0, & 0 \leq t < t_0 \\ \frac{1}{RC} \cdot e^{-\frac{t-t_0}{RC}}, & t \geq t_0 \end{cases} \Rightarrow K(t) = \frac{1}{RC} \cdot e^{-\frac{t}{RC}},$   
 "pulse response."

(c) From (\*) we have  $(\mathcal{L} U_C)(s) = (\mathcal{L} U_0)(s) \cdot (\mathcal{L} K)(s) \Rightarrow$   
 $\Rightarrow U_C(t) = U_0(t) * K(t).$

convolution Then Note:  $\int_0^{\infty} K(t) dt = [-e^{-\frac{t}{RC}}]_0^{\infty} = 1 \Rightarrow U_C$  is a ...

(d)  $R \cdot C = 10 \text{ k}\Omega \cdot 100 \mu\text{F} = 1000 \text{ k}\Omega \cdot \mu\text{F} = 1 \Omega\text{F} = 1 \text{ s}^{-1}?$

$U_0(t) = \cos(\omega t).$

$\Rightarrow U_C(t) = \{ U_0(t) * K(t) = \int_0^t U_0(t-\tau) \cdot K(\tau) d\tau =$

$= \int_0^t \underbrace{\cos(\omega(t-\tau))}_u \cdot \underbrace{e^{-\frac{\tau}{RC}}}_{v'} d\tau \quad \text{Int. by parts.}$

$= [-\cos(\omega(t-\tau)) \cdot e^{-\frac{\tau}{RC}}]_0^t - \int_0^t \underbrace{\sin(\omega(t-\tau))}_u \cdot \underbrace{e^{-\frac{\tau}{RC}}}_{v'} d\tau \quad \text{Int. by parts.}$

$= -e^{-t} + \cos(\omega t) + [-\omega \sin(\omega(t-\tau)) \cdot e^{-\frac{\tau}{RC}}]_0^t - \omega \int_0^t \cos(\omega(t-\tau)) \cdot (-\omega) \cdot (-e^{-\tau}) d\tau$

$= -e^{-t} + \cos(\omega t) + \omega \sin(\omega t) - \omega^2 U_C(t).$

$\Rightarrow U_C(t) = \frac{1}{1 + \omega^2} \cdot (-e^{-t} + \cos(\omega t) + \omega \sin(\omega t))$

for  $t \rightarrow \infty$  oscillation with amplitude of  $\sqrt{1 + \omega^2}$

$\rightarrow$  complete amplitude:  $\frac{1}{1 + \omega^2} \cdot \sqrt{1 + \omega^2} = \frac{1}{\sqrt{1 + \omega^2}}$



The higher the amplitude frequency, the lower the amplitude  $\Rightarrow$  low-pass filter!